

Fundamentals of Computer Architecture

A Review Of Chapters 1 to 7



OVERVIEW

- This presentation includes:
 - Introducing The Processor
 - Fundamental Concepts I - Data Representation
 - Fundamental Concepts II - Digital Electronic Circuits
 - Registers
 - The ALU
 - Buses
 - Memory



Introducing The Processor


- Computer are everywhere
- Definition:
 - It must take *input* of some sort;
 - It must produce *output* of some sort;
 - It must *process* the information somehow;
 - It must have some sort of *information store*;
 - It must have some way of *controlling* what it does.
- Most computers are embedded in other devices





Introducing The Processor

 
- *A von Neumann architecture,*
- We need:
 - A processor - to process information, and to control the system;
 - Memory - for data and instruction storage;
 - Some form of input device;
Some form of output device.







Introducing The Processor

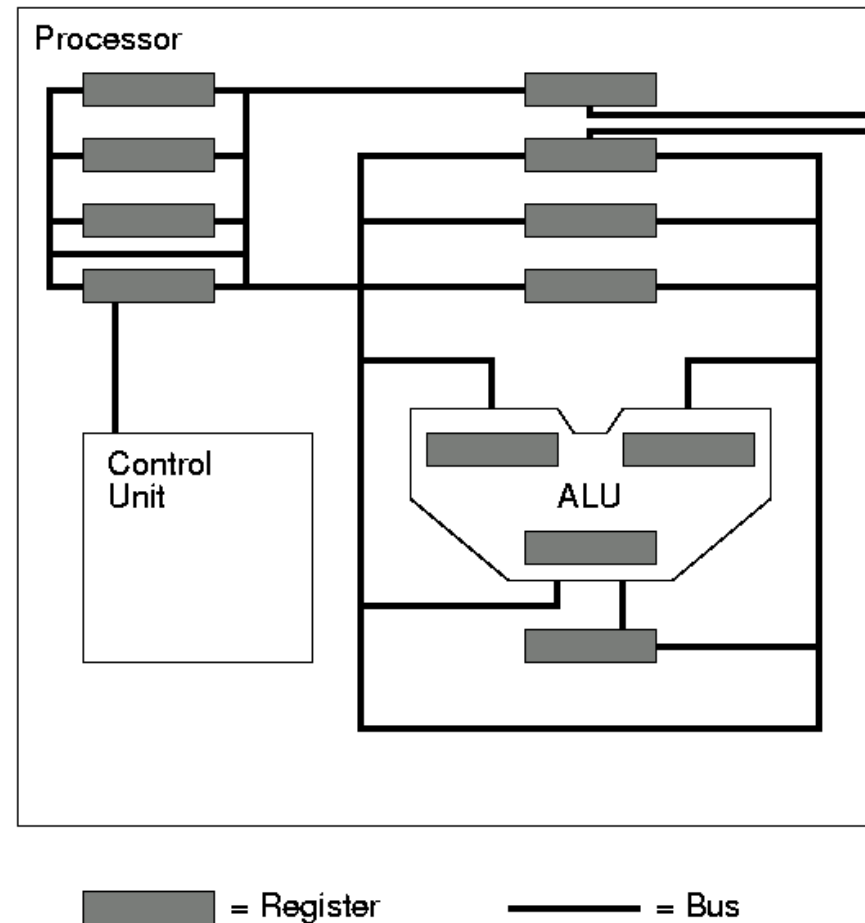- To build our simple processor we need the following components:
 - Some *Registers* - a register is a store where we can place one piece of data;
 - An *Arithmetic Logic Unit*, or *ALU* - a very basic calculator for our processor.
 - A *Control Unit*, or *CU* - to run the processor;
 - Some buses - to allow us to move data from one component to another.





Introducing The Processor

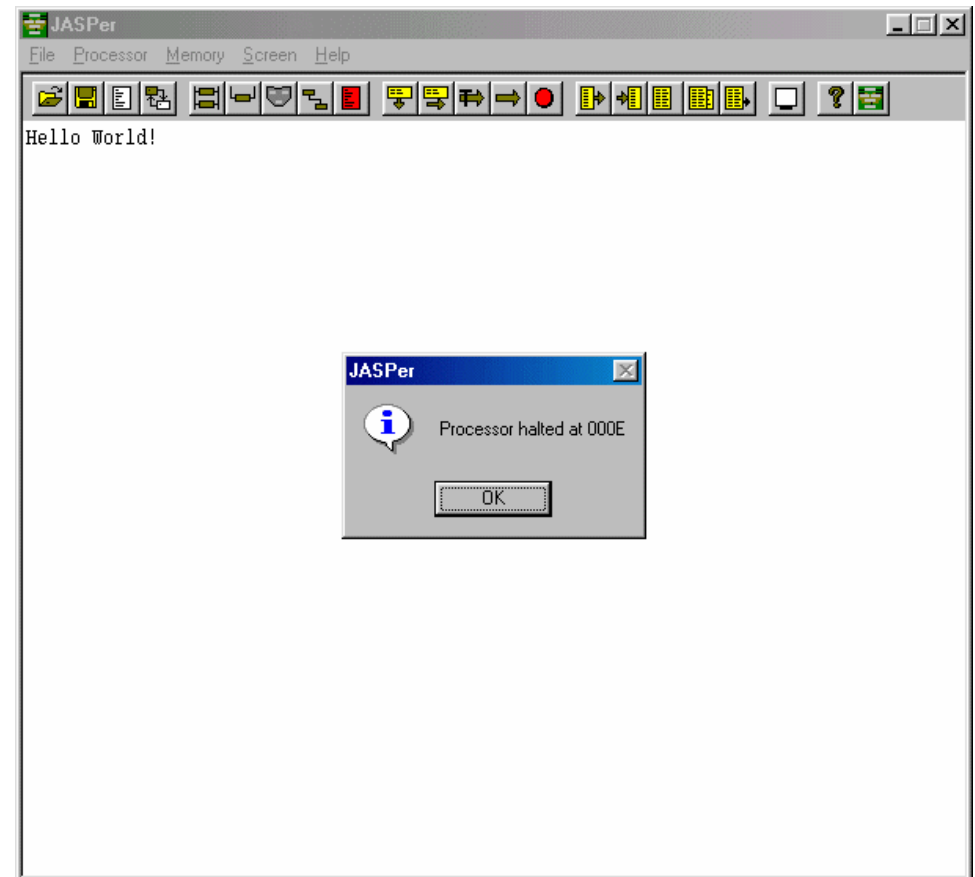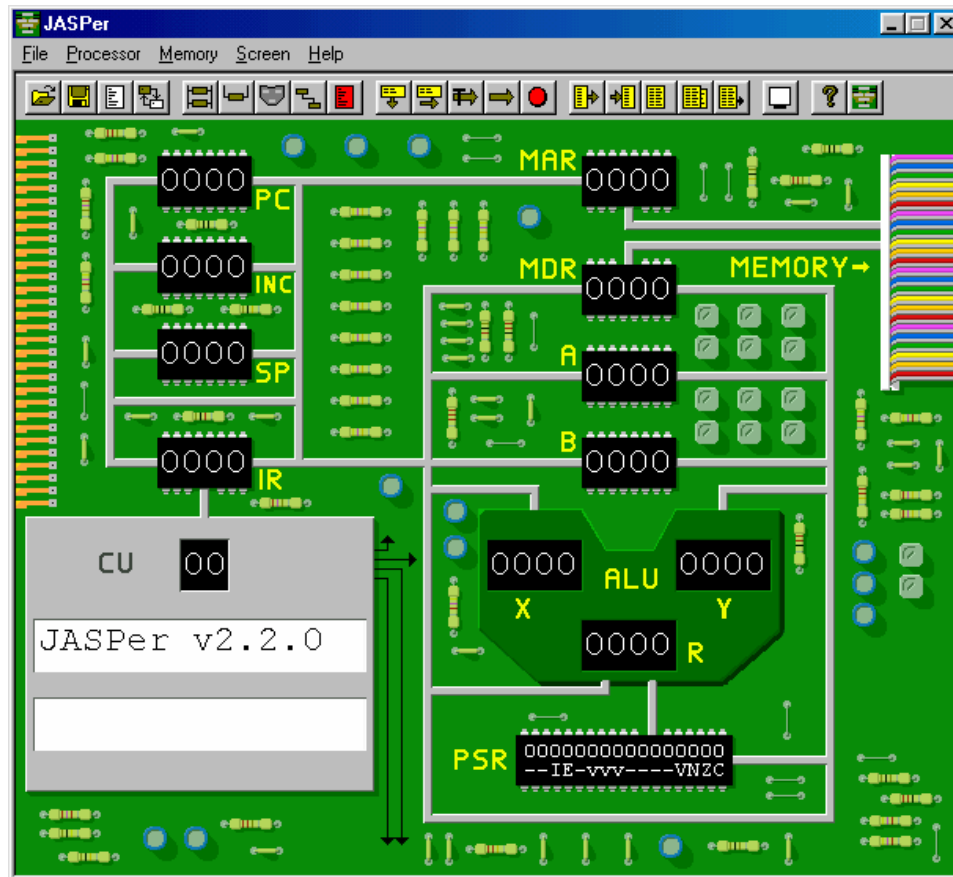



Fundamental Concepts I - Data Representation

- We covered:
 - Number representation - decimal, binary, octal, hexadecimal and Binary Coded Decimal (BCD);
 - Conversion between different bases;
 - Binary arithmetic;
 - Signed representations - sign and modulus, 1's complement, 2's complement and floating point;
 - Logic operations - AND, OR and NOT;
 - Data representation - ASCII and Unicode.



Fundamental Concepts I - Data Representation

- The simple rule for obtaining the 2's complement representation of the negative of a number is
 - Flip the bits
 - Add 1

0 0 0 0 0 1 1 1	Decimal Representation +7
<hr/>	
1 1 1 1 1 0 0 0	Flip the bits
1	Add 1
<hr/>	
1 1 1 1 1 0 0 1	Result represents -7
<hr/>	



Fundamental Concepts I - Data Representation

- Now we know how to figure out the representation of a negative number, let's try some arithmetic

0 0 0 0 0 1 0 1	+	Decimal Representation
1 1 1 1 1 1 0 1		+5
0 0 0 0 0 0 1 0		-3
1 1 1 1 1 1 1		Result
↑		Carries generated
1		Discard final carry



Fundamental Concepts I - Data Representation

$\begin{array}{r} 01011000 \\ 00101001 \\ \hline 10000001 \end{array}$	<p>Decimal Representation +88 +41 Initial result</p>
$1111 \quad \leftarrow$	Carries generated
$\begin{array}{r} 10000001 \\ \hline \end{array}$	Initial result is negative
$\begin{array}{r} 01111110 \\ 1 \\ \hline \end{array}$	Flip the bits Add 1
01111111	Result is therefore -127 ????



Fundamental Concepts I - Data Representation

$$\begin{array}{r} 0010011\boxed{1} \\ 0010111\boxed{0} \\ \hline 0010011\boxed{0} \end{array} \quad \begin{array}{l} X \\ Y \\ X \text{ AND } Y \end{array}$$

$$\begin{array}{r} 0010011\boxed{1} \\ 0010111\boxed{0} \\ \hline 0010111\boxed{1} \end{array} \quad \begin{array}{l} X \\ Y \\ X \text{ OR } Y \end{array}$$


$$\begin{array}{r} 0010011\boxed{1} \\ \hline 1101100\boxed{0} \end{array} \quad \begin{array}{l} X \\ \text{NOT } X \end{array}$$



Fundamental Concepts I - Data Representation

- ASCII
 - For example, the ASCII code for the letter 'R' is found as follows:
 - The column that 'R' is in is labelled with the hexadecimal digit 5;
 - The row that 'R' is in is labelled with the hexadecimal digit 2;
 - This produces the hexadecimal value 52_{16} .
 - ASCII is being replaced by 16-bit **Unicode**.

		High Hexadecimal Digit							
		0	1	2	3	4	5	6	7
Low Hexadecimal Digit	0	NUL	DCL		0	@	P	'	p
	1	SOH	DC1	!	1	A	Q	a	q
	2	STX	DC2	"	2	B	R	b	r
	3	ETX	DC3	#	3	C	S	c	s
	4	EOT	DC4	\$	4	D	T	d	t
	5	ENQ	NAK	%	5	E	U	e	u
	6	ACK	SYN	&	6	F	V	f	v
	7	BEL	ETB	'	7	G	W	g	w
	8	BS	CAN	(8	H	X	h	x
	9	HT	EM)	9	I	Y	i	y
	A	LF	SUB	*	:	J	Z	j	z
	B	VT	ESC	+	;	K	[k	{
	C	FF	FS	,	<	L	\	l	
	D	CR	GS	-	=	M]	m	}
	E	SO	RS	.	>	N	^	n	~
	F	SI	US	/	?	O	_	o	DEL

 


Fundamental Concepts II - Digital Electronic Circuits

- We covered:
 - Gate logic - AND, OR and NOT;
 - How to build circuits with gates;
 - Modelling circuits with truth tables;
 - Boolean algebra, including De Morgan's laws.



Fundamental Concepts II - Digital Electronic Circuits


X	Y	R
0	0	0
0	1	0
1	0	0
1	1	1

 

X	Y	R
0	0	0
0	1	1
1	0	1
1	1	1




X	R
0	1
1	0

 




Fundamental Concepts II - Digital Electronic Circuits


X	Y	R
0	0	1
0	1	1
1	0	1
1	1	0

 


NAND

 

X	Y	R
0	0	1
0	1	0
1	0	0
1	1	0

 


NOR

 

X	Y	R
0	0	0
0	1	1
1	0	1
1	1	0




XOR

 



 Fundamental Concepts II - Digital Electronic Circuits



X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- A circuit diagram can be derived from a truth table



Fundamental Concepts II - Digital Electronic Circuits

- **Boolean Algebra**
 - The set of rules that we can make use of are known as the **identities of boolean algebra**.
- Each identity (apart from the **absorbtion** and **double complement**) has two forms, one for the AND form, and the other for the OR form.

Law	Identity
Absorbtion	$x \cdot (x + y) = x$
Associative	$x + (y + z) = (x + y) + z$ $x \cdot (y \cdot z) = (x \cdot y) \cdot z$
Complement	$x + \bar{x} = 1$ $x \cdot \bar{x} = 0$
Commutative	$x + y = y + x$ $x \cdot y = y \cdot x$
De Morgan's Laws	$\overline{(x \cdot y)} = \bar{x} + \bar{y}$ $\overline{(x + y)} = \bar{x} \cdot \bar{y}$
Distributive	$x + (y \cdot z) = (x + y) \cdot (x + z)$ $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
Dominance	$x + 1 = 1$ $x \cdot 0 = 0$
Double Complement	$\overline{(\bar{x})} = x$
Idempotent	$x + x = x$ $x \cdot x = x$
Identity	$x + 0 = x$ $x \cdot 1 = x$




Fundamental Concepts II - Digital Electronic Circuits

- Boolean Algebra
 - De Morgan's Laws can help us in the creation of *efficient* digital circuits.

$$\overline{(x \cdot y)} = \bar{x} + \bar{y}$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

Gate	Number of transistors
AND	3
OR	3
NOT	1
NAND	2
NOR	2

 

Registers


- We covered:
 - Bistables - the RS latch, the D latch and the D flip-flop;
 - How to build a register;
 - Tri-state logic;
 - The concept of a clock and a clock cycle.



Registers

The RS Latch

R	S	Description
0	0	Q is left at what it was previously set to
0	1	$Q = 1$
1	0	$Q = 0$
1	1	$Q = \bar{Q} = 0$

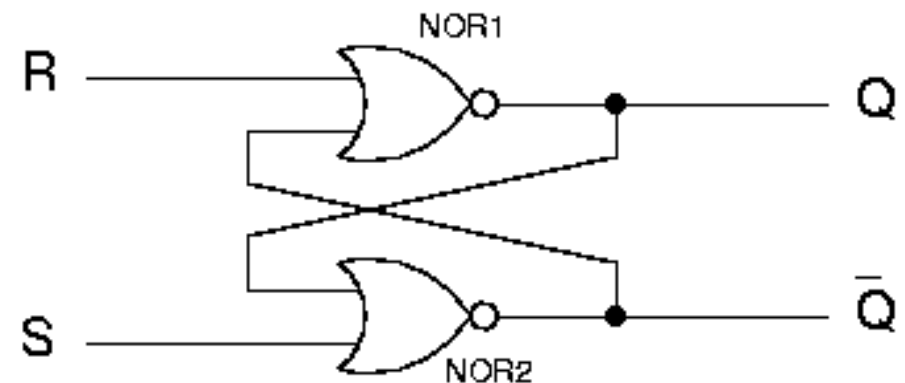





Registers

The D Latch



D	C	Description
0	0	Q is left at what it was previously set to.
0	1	Q = 0
1	0	Q is left at what it was previously set to.
1	1	Q = 1

 


 

Registers


The D Flip-flop

  

 


Registers

A 4-bit register

 


A 4-bit register attached to a bus

 



Registers

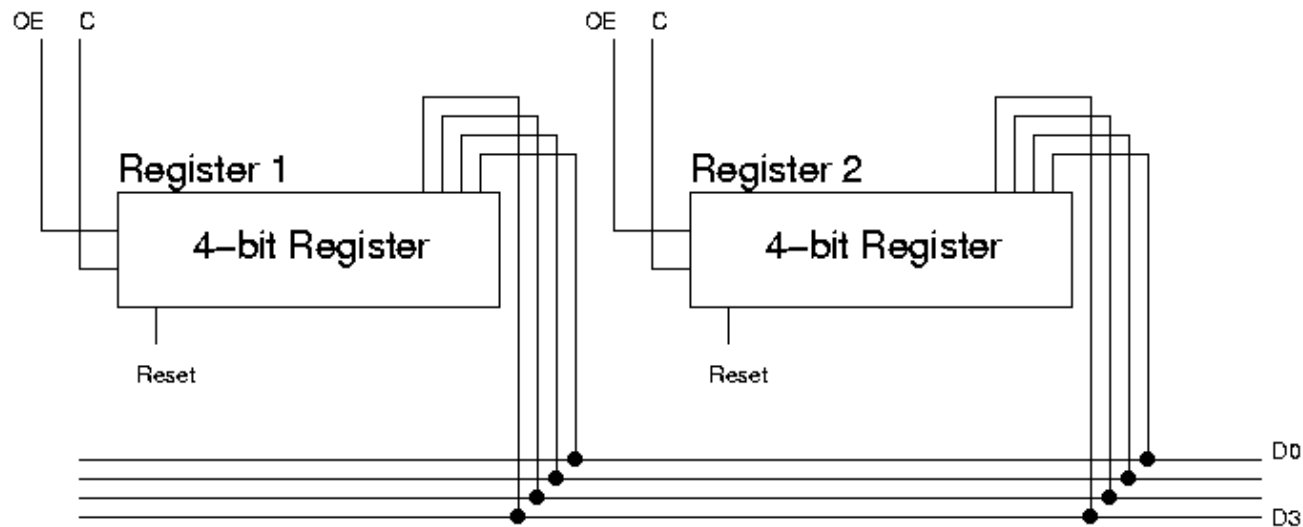


- To move a bit pattern from register 1 to register 2 we would do as before:
 - Set register 1 OE to 1 (bit pattern now on the bus);
 - Clock register 2 (for register 2 to take the bit pattern from the bus);
 - Set register 1 OE to 0;



Registers

 - The Clock cycle
- There are effectively four different types of trigger. These are:
 - 1 triggered - when the clock signal becomes 1;
 - 0 triggered - when the clock signal becomes 0;
 - Positive edge triggered - when the clock signal changes from a 0 to a 1;
 - Negative edge triggered - when the clock signal changes from a 1 to a 0.







The ALU

- We covered:
 - The role of the ALU and PSR within the processor;
 - The control circuitry of the ALU;
 - Adder circuits - the half adder and the full adder;
 - Building circuits to demonstrate the functionality of the ALU – the ADD, SL and NEG circuits.




The ALU

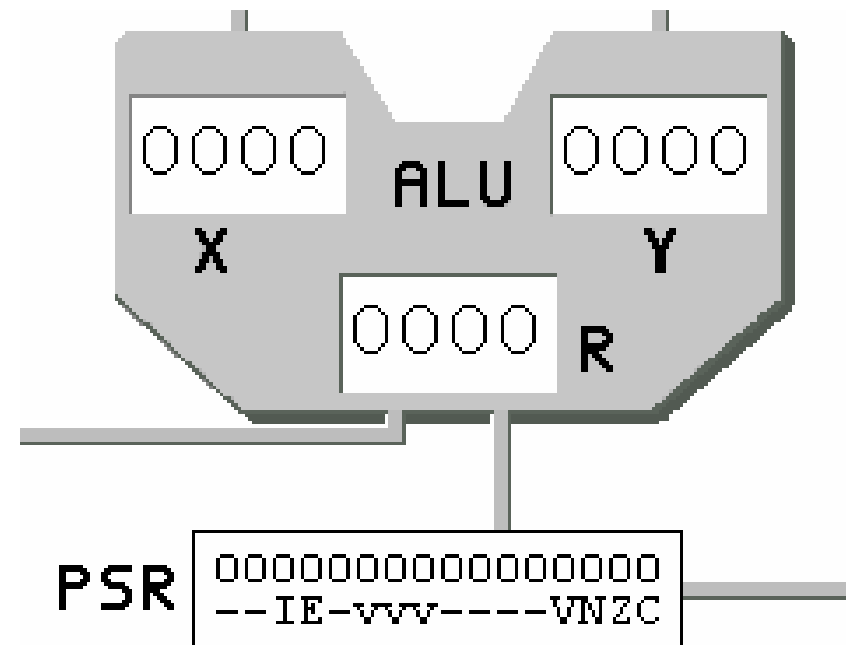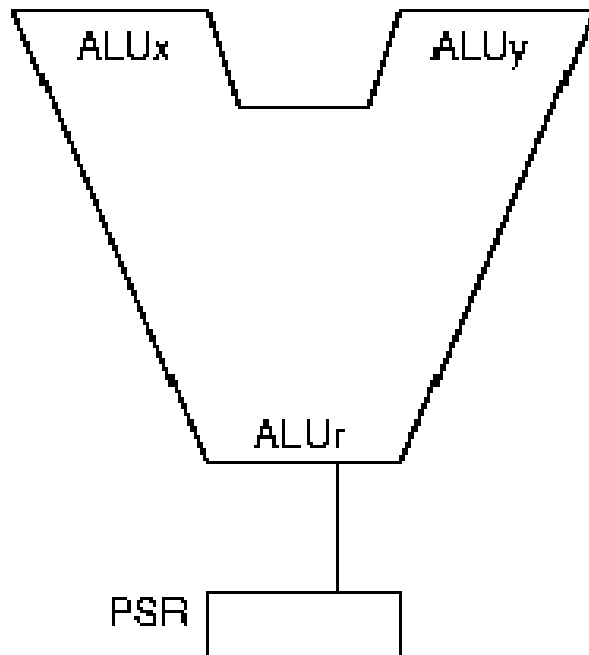




The ALU

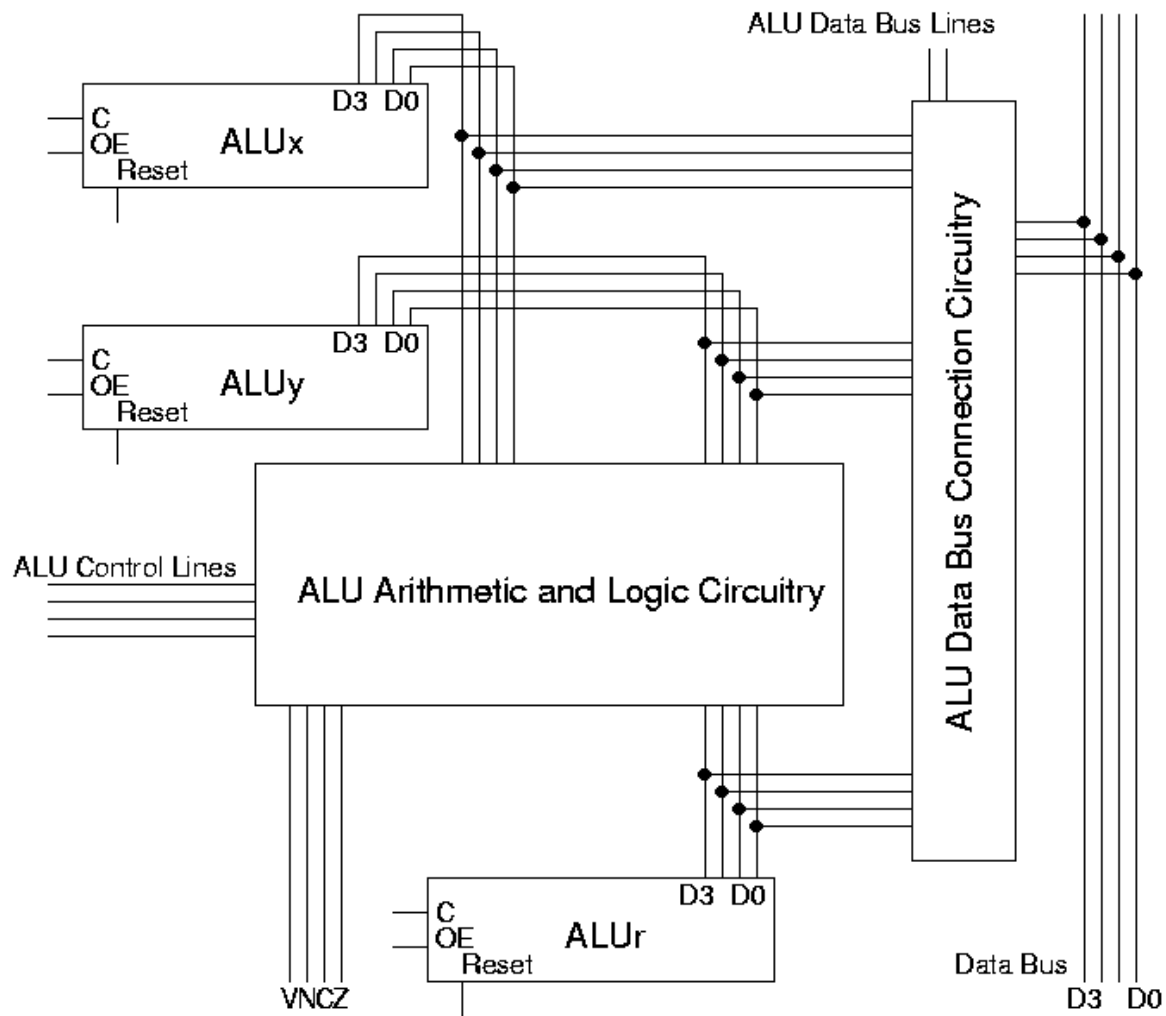




The ALU

Half Adder

 


Full Adder

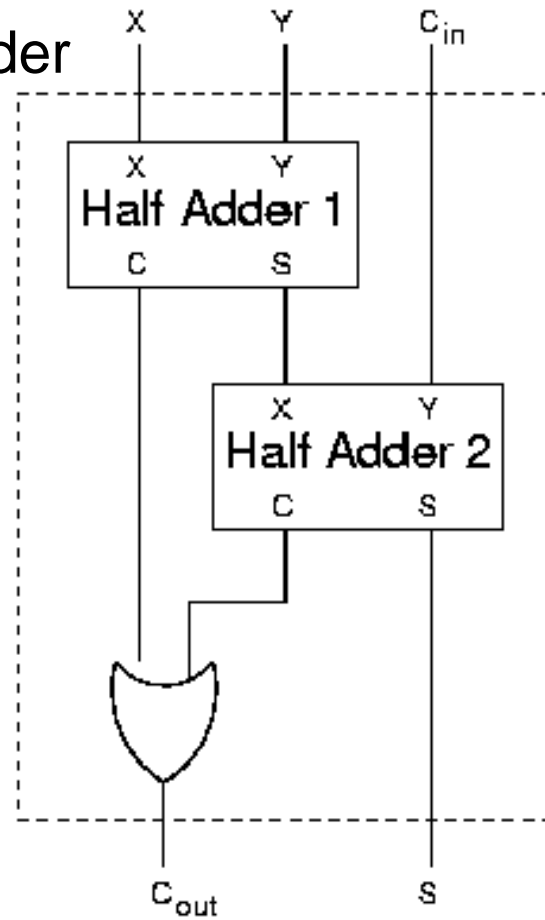



The ALU

The ADD circuit

 




Buses

- We covered:
 - Processor buses - the data bus, the address bus and the control bus;
 - Building a bus with gate logic;
 - Timing diagrams.




Buses

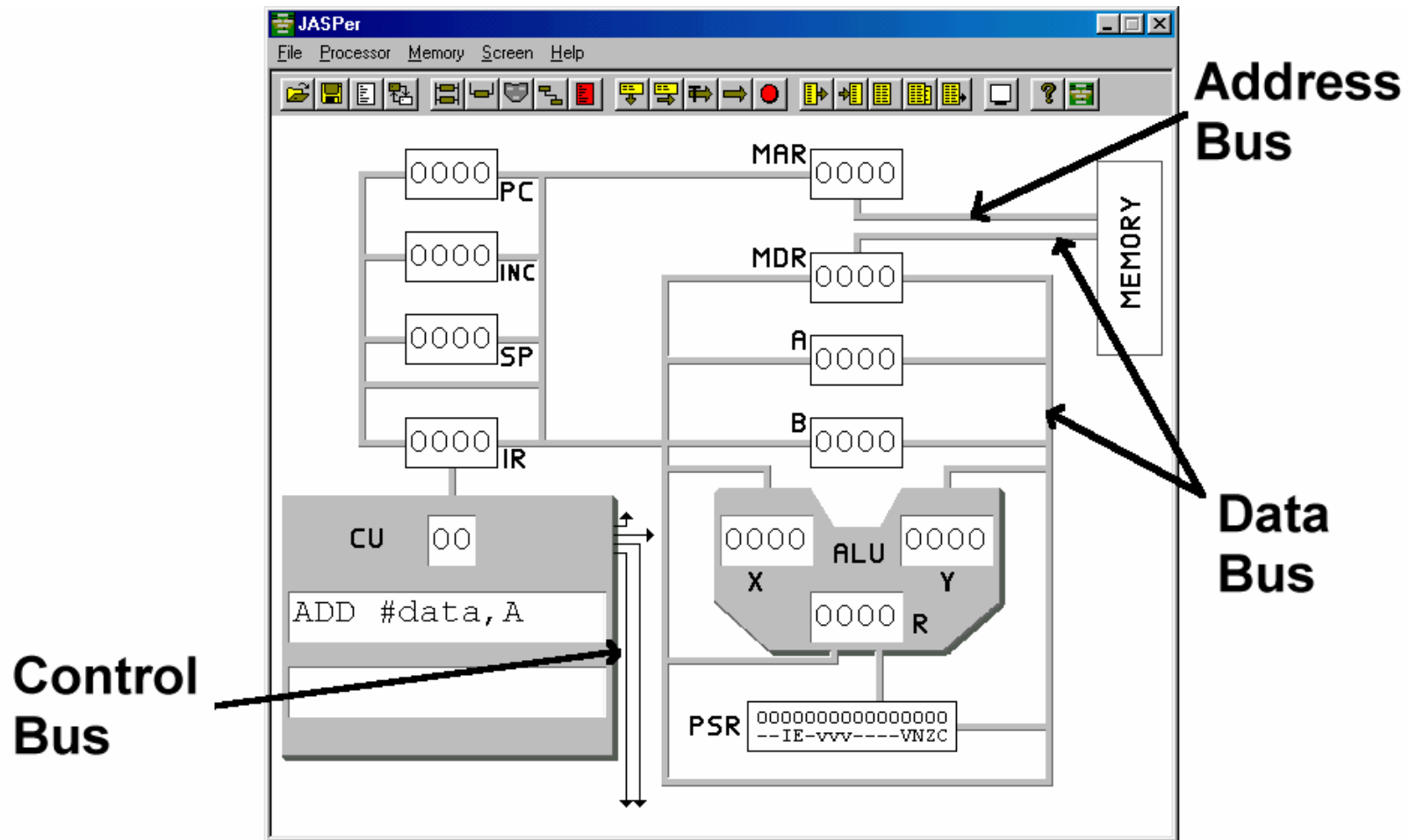



Buses

A timing diagram

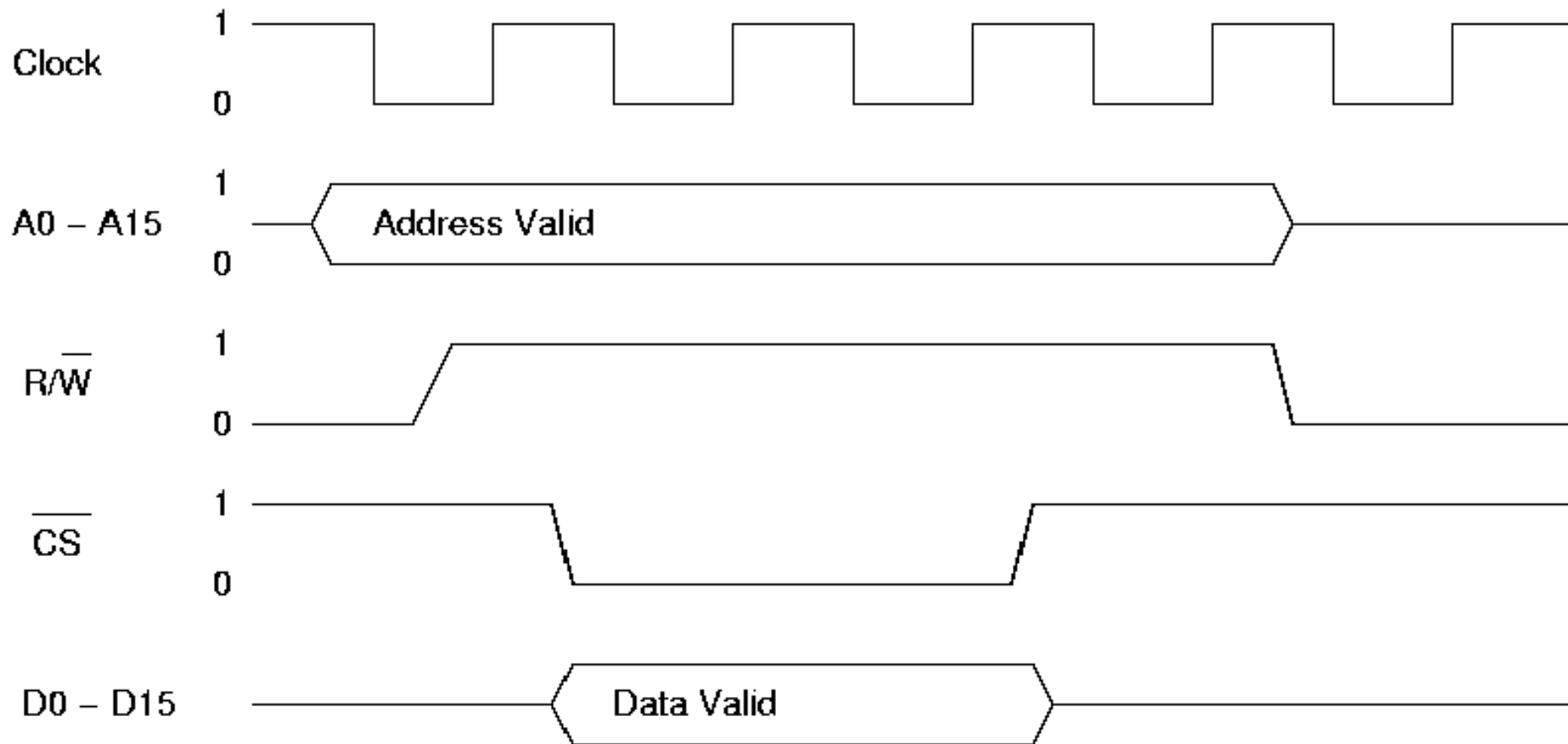



Memory

- We covered:
 - The concepts of memory;
 - How to build memory from gate logic;
 - Types of memory;
 - Address decoding strategies;
 - Memory maps.



Memory

A small memory

Memory Width


←————→

00	1	1	0	0
01	0	1	0	1
10	0	0	0	1
11	0	1	1	0

Storage Size


↑————↓

A D flip-flop

 





Memory

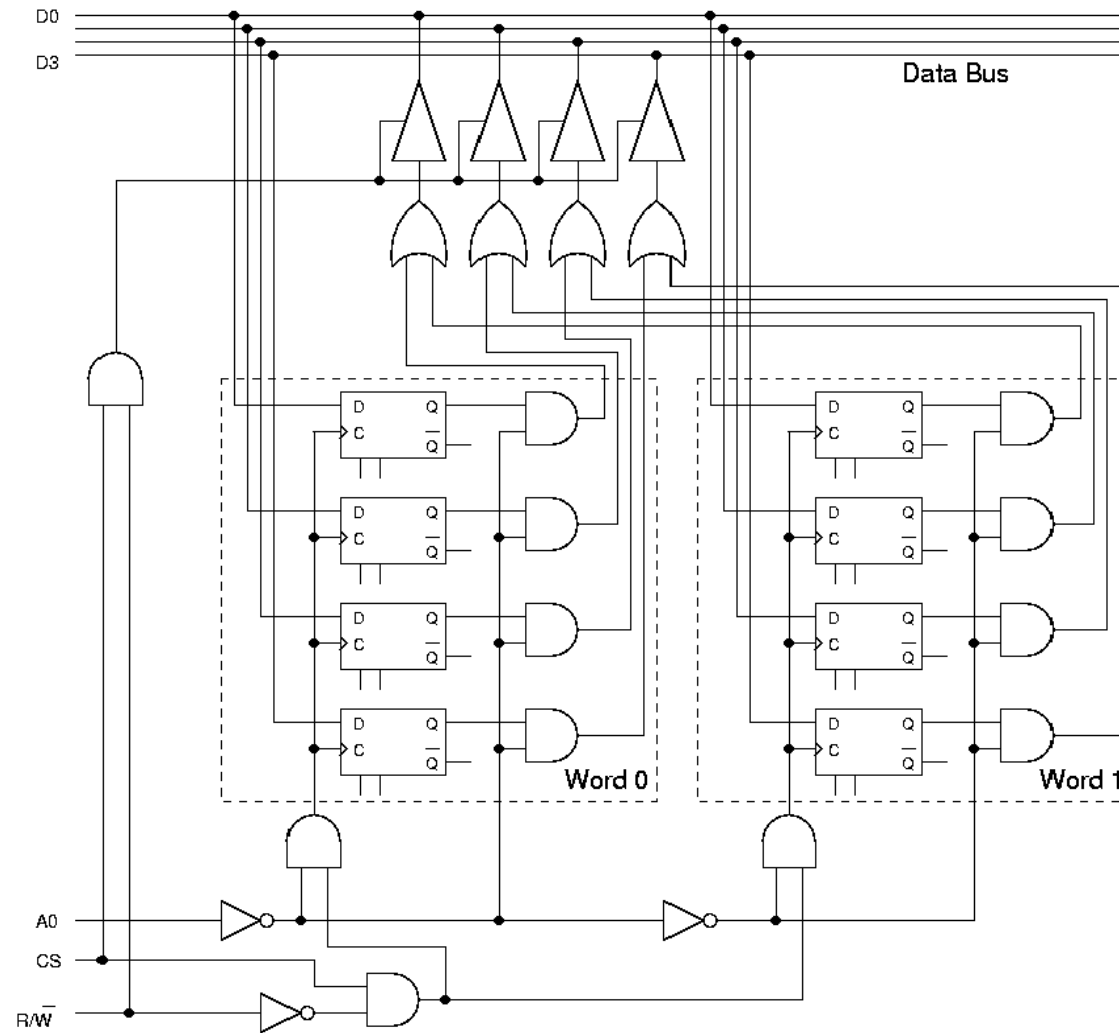




Memory

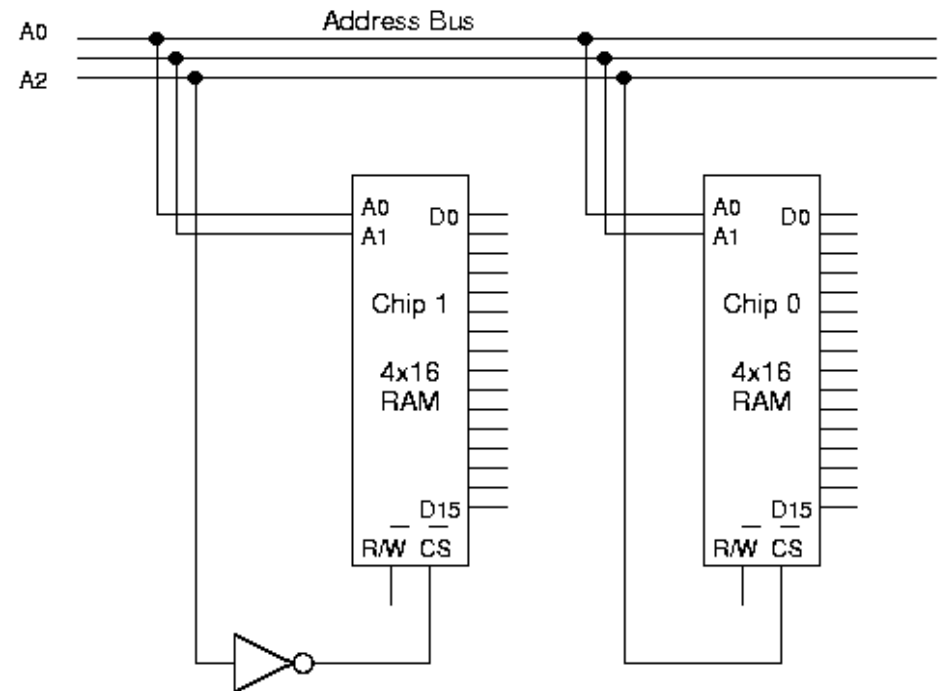 




Memory

Building wider memories

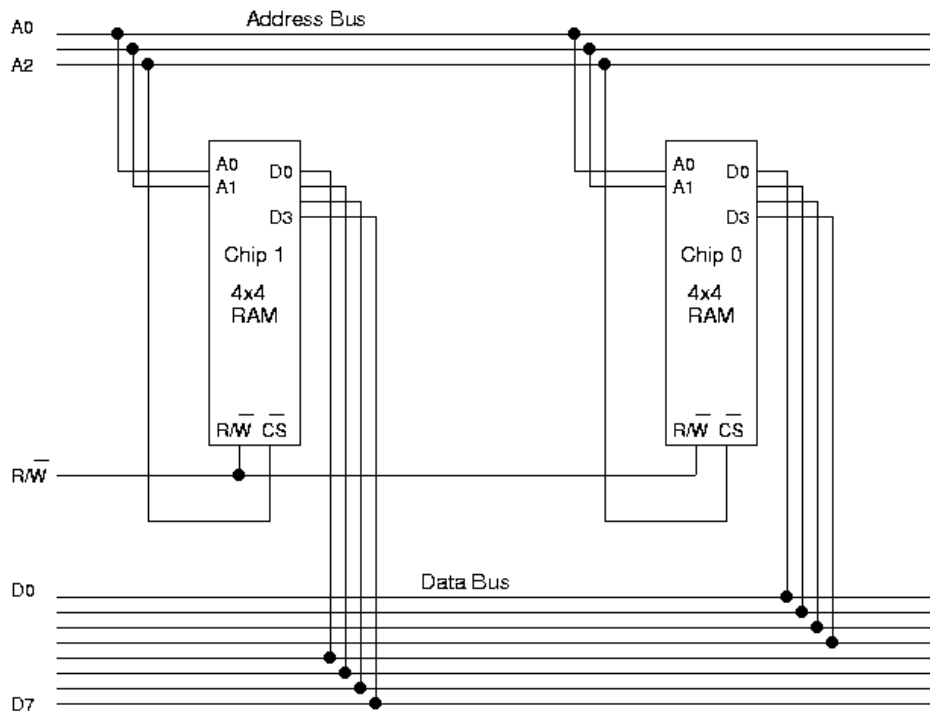

Partial address mapping

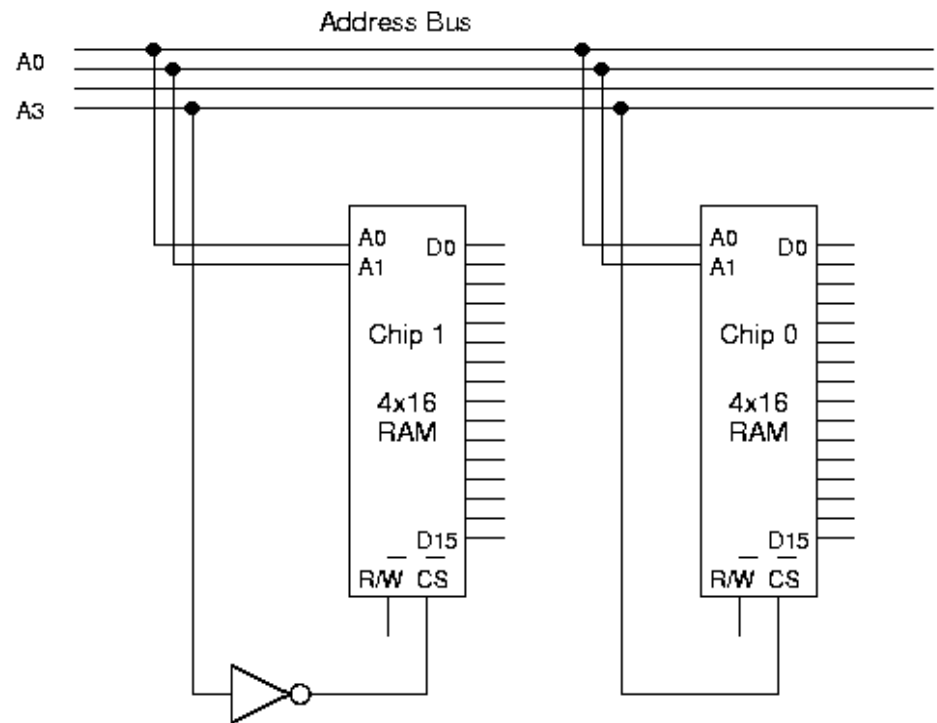



Memory

JASPer memory

```

Memory
0000:9005 MOVE #data,A
0001:9103 MOVE #data,B
0002:0600 ADD B,A
0003:F000 HALT
0004:0000 ADD #data,A
0005:0000 ADD #data,A
0006:0000 ADD #data,A
0007:0000 ADD #data,A
0008:0000 ADD #data,A
0009:0000 ADD #data,A
000A:0000 ADD #data,A
000B:0000 ADD #data,A
000C:0000 ADD #data,A
000D:0000 ADD #data,A
000E:0000 ADD #data,A
000F:0000 ADD #data,A
  
```

OK

